

# Single-Supply Applications of CMOS MICRODACs

National Semiconductor  
Application Note 284  
Tim Regan  
September 1981




Single-Supply Applications of CMOS MICRODACs

CMOS data acquisition and conversion products are becoming the ideal choice for microprocessor controlled analog systems. The use of CMOS allows the addition of more digital logic functionality on to the same die as the analog circuitry to minimize external parts requirements. The inherently low power consumption is also a big factor for battery operation and low heat generation in large scale systems.

National's MICRODAC™ family of 8, 10 and 12-bit D to A converters all feature on-chip data latches to permit direct interface to 8 or 16-bit data busses. These devices were designed to provide the most versatility from an analog standpoint. By utilizing a current switching R-2R ladder network (Figure 1), the applied reference voltage can be either a stable DC voltage or an AC voltage within the wide range of  $\pm 10V$ . However, output linearity requires that the two current output terminals be biased to 0V. This is accomplished by using an external op amp to serve as a current-to-voltage converter. Negative feedback via the feedback resistor included in the DAC keeps the  $I_{OUT1}$  terminal at a virtual ground potential. A drawback to this technique is that the output amplifier inverts and outputs a voltage of the opposite polarity of the applied reference. This then requires the output amplifier to have a negative supply voltage if the reference were positive. To operate with only a single-supply by biasing the ground pin of the DAC and the inputs of the op amp to  $\frac{1}{2}$  the supply does not work, as the digital inputs are no longer TTL compatible.

All hope is not lost, however, if single-supply operation is essential. By taking a somewhat backwards view of the DAC ladder network, only a single positive supply is necessary. In Figure 2 the R-2R ladder network is used to switch voltages rather than currents.<sup>1</sup> By applying the reference to the normal current output terminal ( $I_{OUT1}$ ) and grounding  $I_{OUT2}$  the voltage at the reference terminal will be a fraction of the reference voltage and a function of the applied digital input code.


There are two important considerations when using this voltage-switching approach. The applied reference voltage must be positive since there are internal parasitic diodes from the  $I_{OUT}$  terminals to ground which would turn on if the reference were to be negative. This, of course, is of no concern with single-supply applications. There is also a dependence of converter linearity and gain error on the voltage difference between the DAC's  $V_{CC}$  supply and the applied reference voltage. This is a result of the voltage drive requirement of the CMOS ladder switches. To ensure that all of the switches can turn on sufficiently (so as not to add significant resistance to any leg of the ladder and thereby introduce additional linearity and gain errors) an 8-bit DAC should not have a reference greater than 5V and the  $V_{CC}$  supply should be at least 9V more positive than the reference. This would keep linearity and gain error degradation less than 0.1%. A 10-bit DAC is a bit more stringent. For a 0.005% or less error degradation, the reference should be less than  $3 V_{DC}$  and  $V_{CC}$  should be 10V more positive. The typical effects of bringing  $V_{REF}$  and  $V_{CC}$  closer together,

 

N = Number of bits of resolution

TL/H/5633-6

FIGURE 1. The Standard Current-Switching R-2R Ladder Network

 

TL/H/5633-1

FIGURE 2. Operating the Ladder "Backwards" to Serve as a Voltage-Switching Network

MICRODAC™ is a Trademark of National Semiconductor Corp.

as well as temperature performance, are shown graphically in *Figure 3* for the 8-bit DAC0830 series.

Since the output is now a voltage rather than a current, an output op amp is not necessarily required, but the DAC's output impedance is fairly high (equal to its specified reference input resistance of 10k to 20k), so an op amp may be required for buffering purposes. *Figure 4* shows a single-supply DAC with an output amplifier providing buffering and gain for a more useful 0V to 10V output from a 2.5V reference. The LM336 reference diode is biased through the internal feedback resistor between the I<sub>OUT1</sub> pin and the R<sub>fb</sub> pin. The zero-code output voltage is limited by the lower output saturation voltage of the LM358 op amp. The 2k pull-down load resistor helps to reduce this voltage to 10 mV or 1/4 of an output LSB. Even with a 15V DAC supply, the digital inputs remain T<sup>2</sup>L compatible.


Closer inspection of *Figure 2* shows that both I<sub>OUT1</sub> and I<sub>OUT2</sub> drive the ladder network in an identical manner. Each leg is connected to either I<sub>OUT1</sub> or I<sub>OUT2</sub> as controlled by the logic state of each digital input. If each I<sub>OUT</sub> terminal is biased to separate reference potentials, the circuit of *Figure*

5 results. This is a single-supply DAC with an adjustable zero-code output offset voltage and adjustable output span to reserve the full resolution of the DAC for a range of voltages other than 0V to full-scale. An important point to note is that for an all ones code applied, only the voltage at I<sub>OUT1</sub> is connected to the ladder and sets the output to 255/256 times the voltage of I<sub>OUT1</sub>. With an all zeros code applied, only the voltage at I<sub>OUT2</sub> drives the ladder, setting the output to 255/256 times this voltage. This non-interaction of the two inputs at the end-points makes calibration a breeze. The incremental analog output steps are automatically set to (V<sub>MAX</sub> - V<sub>MIN</sub>)/256.

The buffers at the two reference inputs in *Figure 5* isolate the code-dependent resistance to ground at I<sub>OUT1</sub> and I<sub>OUT2</sub> from the resistive string used to set V<sub>MAX</sub> and V<sub>MIN</sub>. The output responds in accordance to the following expression.

$$(1) \quad V_{OUT} = D/256 (V_{MAX} - V_{MIN}) + 255/256 V_{MIN}$$

 Where D is the decimal equivalent of the 8-bit binary control word.



Note: For these curves, V<sub>REF</sub> is the voltage applied to the I<sub>OUT1</sub> terminal and I<sub>OUT2</sub> is grounded.

FIGURE 3. The Effects of Bringing the V<sub>CC</sub> Supply and V<sub>REF</sub> Closer Together and Temperature Performance Using the DAC in the Voltage-Switching Mode

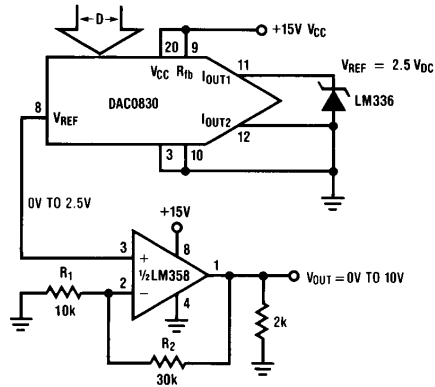


FIGURE 4. Obtaining 0V to 10V Output from a 2.5V Reference

 


FIGURE 5. A Single-Supply DAC with Level Shift and Span Adjustable Output

A common requirement of single-supply systems is that the outputs of signal-conditioning amplifiers must be DC biased, typically to  $\frac{1}{2}$  of the  $V_{CC}$  supply, to provide maximum unclipped AC signal swing. The circuit of Figure 6 shows how this dual-input voltage-switching DAC configuration can allow the digital input code to control the attenuation of an AC signal without significantly affecting the DC biasing level. If the voltage at  $I_{OUT2}$  is set to the DC level of the voltage at  $I_{OUT1}$ , then the term in equation (1) which is controlled by the digital input code, D, reduces to just the AC signal at  $I_{OUT1}$ . The DC level at the output is 255/256 times the DC level at the input.

The circuit of Figure 7 combines the advantages of low power consumption of the CMOS MICR0DACs together with the non-interactive zero and full-scale adjustability of this voltage-switching technique. This circuit is an isolated 4 mA-20 mA current loop controller where the DAC sets the

amount of current that flows through the loop, yet receives its own power from the very same loop.

Digital control and isolation are provided by a single optoisolator and a CMOS counter. The controlling processor must generate a clock and keep track of the number of clock pulses issued to the circuit to know what the loop current is at any time. On power-up the counter is reset to all zeros to give the processor a starting point, as well as to inherently provide a calibration point. When calibrating, potentiometer P1 would be set for the zero-code loop current of 4 mA. The processor would then issue exactly 255 clock pulses to the opto-isolator. Potentiometer P2 can then adjust the full-scale current value to 19.92 mA. If one more clock pulse is issued, the DAC input code returns to all zeros and the previously set value of 4 mA will flow, as this setting was unaffected by the full-scale adjustment.

 


FIGURE 6. Single-Supply DAC where the Digital Input Word Affects the Attenuation of an AC Signal without Significantly Altering its DC Biasing Level

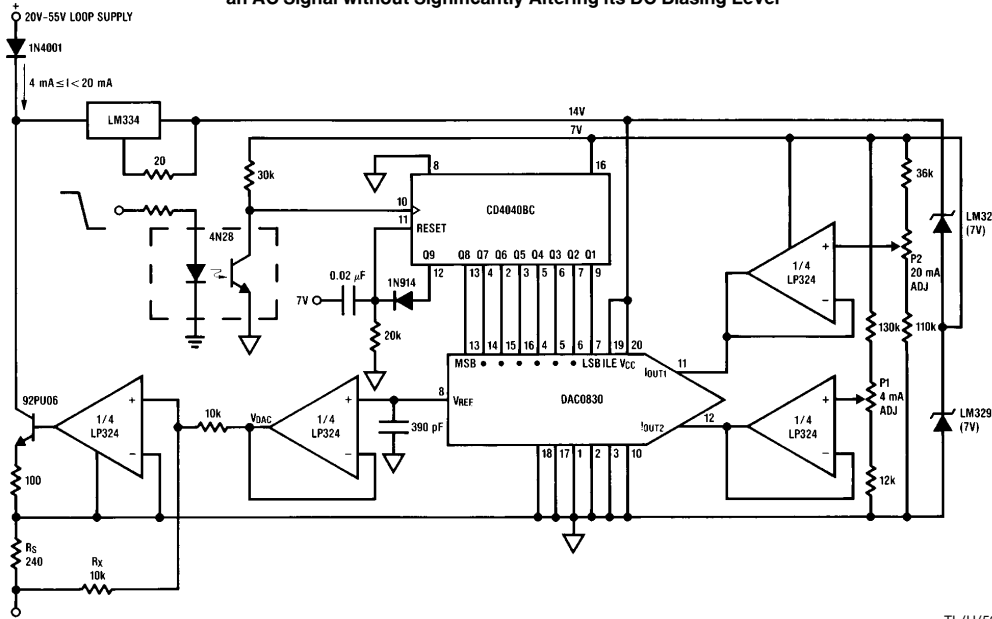


FIGURE 7. Easily Calibrated, Isolated 4 mA-20 mA Current Loop Controller

TL/H/5633-4

The NPN emitter-follower will conduct whatever level of current necessary to keep the voltage across resistor  $R_S$  equal to the voltage across resistor  $R_X$ . This voltage is equal to the output voltage at the  $V_{REF}$  pin of the DAC which can be determined from equation (1). The actual loop current is:

$$(2) I_{LOOP} = V_{DAC} / (R_S + 1/R_X)$$

The second LM329 reference diode is used to bias the DAC  $V_{CC}$  supply higher than the voltages at  $I_{OUT1}$  and  $I_{OUT2}$  to preserve linearity.

Finally, what if a D to A function is required, but only a single 5V supply is available and minimal supply current is a primary concern (battery powered instrumentation is a good example)? The voltage-switching techniques previously described are not suitable because not enough voltage is available to properly bias the DAC. A CMOS DAC is still attractive for its low supply current requirements and if it can be operated in the standard current switching configuration, a single 5V supply is sufficient. But how about the voltage inversion and the requirement for negative supply potential?

By taking advantage of an age-old technique of clocking a diode-capacitor network connected as a DC to DC voltage inverter, a low current negative supply can be generated. In the circuit of *Figure 8*, 2 diodes and 2 capacitors are clocked by a CMOS Schmitt trigger oscillator and connected in such a fashion as to generate a  $-3.8V$  supply potential. This negative supply is used only to bias a low current LM385-2.5V reference diode to provide the DAC with a stable neg-


ative reference. Now the inversion of the output current-to-voltage converter will generate a positive output ranging from 0V to 2.5V as a function of the digital input code.

The amount of ripple that may appear at the reference input is a function of the dynamic impedance of the LM385, the clock frequency and the size of the switching capacitors. For the component values shown, the clock frequency is approximately 1 kHz and the ripple on the reference is 7 mV peak to peak. This ripple is cleanly filtered by the bypass cap around the feedback resistor of the output amplifier. The output op amp is part of a new low power quad, the LP324, which is ideal for its ability to common-mode to ground on the inputs and swing very close to ground at its output. If an extra CMOS Schmitt inverter is not readily available, the oscillator function can be implemented with another of the amplifiers in the op amp package. The total supply current of this single-supply DAC is on the order of 1.5 mA with no output load.

With this technique even the 12-bit DAC1230 can be used with no linearity degradation which would be apparent in the voltage-switching techniques.

**REFERENCE**

1. Sevastopoulos, N.; Cecil, J.; and Fredericksen, T., "An Unusual Circuit Configuration Improves CMOS-MDAC Performance", EDN Magazine, March 5, 1979, pg. 77.

 

**FIGURE 8. Single 5V Supply, 8-Bit CMOS DAC**

TL/H/5633-5

**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
 1111 West Bardin Road  
 Arlington, TX 76017  
 Tel: (800) 272-9959  
 Fax: (800) 737-7018

**National Semiconductor Europe**  
 Fax: (+49) 0-180-530 85 86  
 Email: cnjwge@tevm2.nsc.com  
 Deutsch Tel: (+49) 0-180-530 85 85  
 English Tel: (+49) 0-180-532 78 32  
 Français Tel: (+49) 0-180-532 93 58  
 Italiano Tel: (+49) 0-180-534 16 80

**National Semiconductor Hong Kong Ltd.**  
 19th Floor, Straight Block,  
 Ocean Centre, 5 Canton Rd.  
 Tsimshatsui, Kowloon  
 Hong Kong  
 Tel: (852) 2737-1600  
 Fax: (852) 2736-9960

**National Semiconductor Japan Ltd.**  
 Tel: 81-043-299-2309  
 Fax: 81-043-299-2408

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.