

# 17. Semiconductor Memories



## Overview

- Introduction
- Read Only Memory (ROM)
- Nonvolatile Read/Write Memory (RWM)
- Static Random Access Memory (SRAM)
- Dynamic Random Access Memory (DRAM)
- Summary

# Semiconductor Memory Classification

Non-Volatile Memory		Volatile Memory	
Read Only Memory (ROM)	Read/Write Memory (RWM)	Read/Write Memory	
Mask-Programmable ROM Programmable ROM	EPROM E <sup>2</sup> PROM FLASH	Random Access	Non-Random Access
		SRAM DRAM	FIFO LIFO Shift Register

EPROM - Erasable Programmable ROM

SRAM - Static Random Access Memory


E<sup>2</sup>PROM - Electrically Erasable Programmable ROM

DRAM - Dynamic Random Access Memory

FIFO - First-In First-Out

LIFO - Last-In First-Out
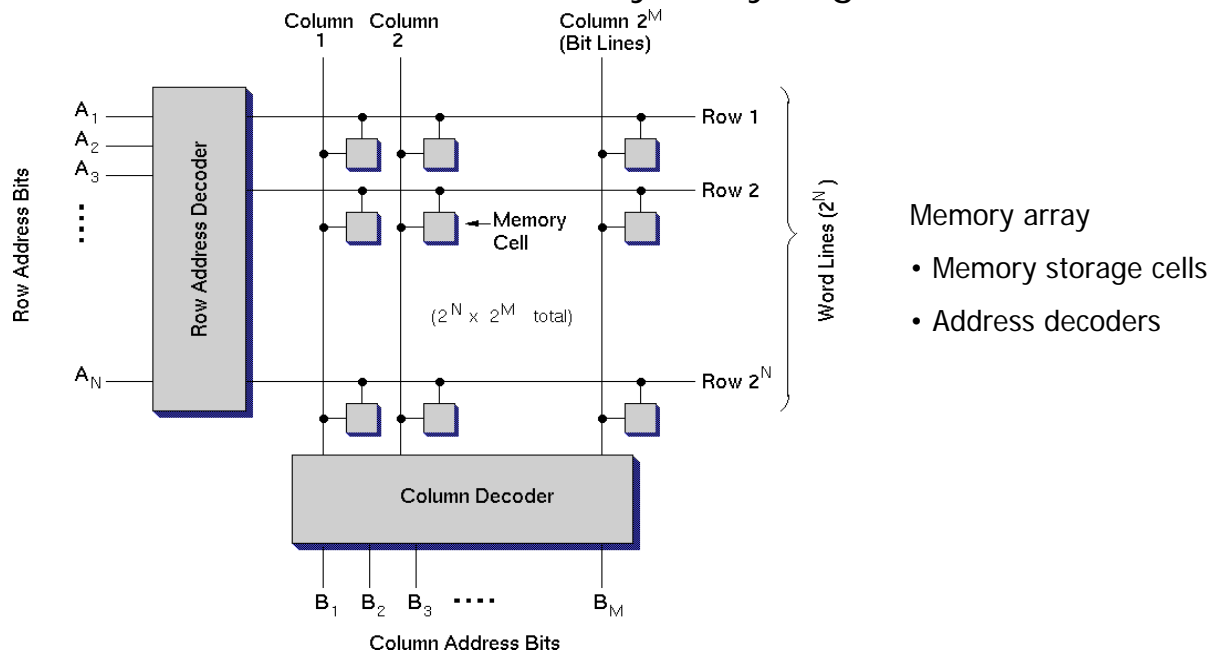
## Random Access Memory Array Organization




Each memory cell

- stores one bit of binary information ("0" or "1" logic)
- shares common connections with other cells: rows, columns

# Read Only Memory - ROM

- Simple combinatorial Boolean network which produces a specific output for each input combination (address)
  - "1" bit stored - absence of an active transistor
  - "0" bit stored - presence of an active transistor
- Organized in arrays of  $2^N$  words
- Typical applications:
  - store the microcoded instructions set of a microprocessor
  - store a portion of the operation system for PCs
  - store the fixed programs for microcontrollers (firmware)

## Mask Programmable NOR ROM (1)

 

- "1" bit stored - absence of an active transistor
- "0" bit stored - presence of an active transistor


Function Table

R1	R2	R3	R4	C1	C2	C3	C4
1	0	0	0	0	1	0	1
0	1	0	0	0	0	1	1
0	0	1	0	1	0	0	1
0	0	0	1	0	1	1	0

NOR ROM with 4-bit words

- Each column  $C_i$  (NOR gate) corresponds to one bit of the stored word
- A word is selected by rising to "1" the corresponding wordline
- All the wordlines are "0" except the selected wordline which is "1"


## Mask Programmable NOR ROM (2)

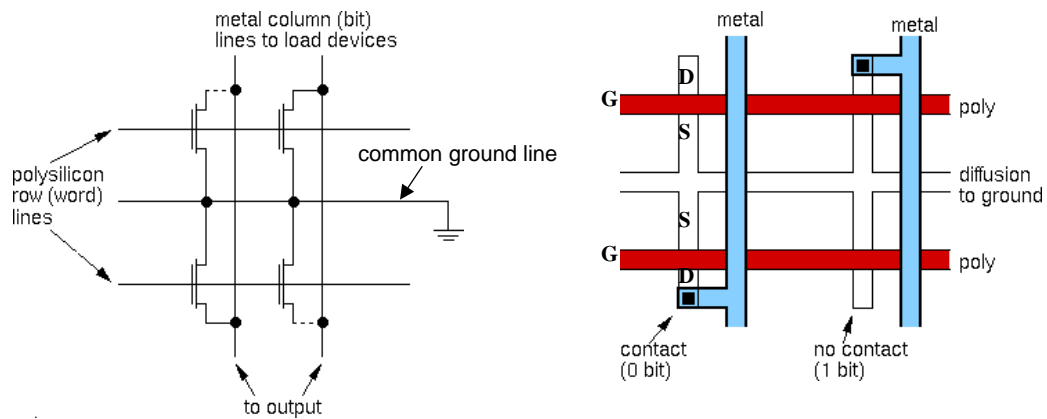

- "1" bit stored - the drain/source connection (or the gate electrode) are omitted in the final metallization step
- "0" bit stored - the drain of the corresponding transistor is connected to the metal bit line

➡ Cost efficient, since few masks have to be manufactured only

## Implant Mask Programmable NOR ROM

 


Idea: deactivation of the NMOS transistors by raising their threshold voltage above the  $V_{OH}$  level through channel implants

- "1" bit stored - the corresponding transistor is **turned off** through channel implant
- "0" bit stored - non-implanted (normal) transistors

Advantage: higher density (smaller area)!

# Implant Mask Programmable NAND ROM (1)

 

- "1" bit stored - presence of a transistor that can be switched off
- "0" bit stored - shorted/normally-on transistor


R1	R2	R3	R4	C1	C2	C3	C4
0	1	1	1	0	1	0	1
1	0	1	1	0	0	1	1
1	1	0	1	1	0	0	1
1	1	1	0	0	1	1	0

NAND ROM with 4-bit words

- Each column  $C_i$  (NAND gate) corresponds to one bit of the stored word
- A word is selected by putting to "0" the corresponding wordline  $R_i$
- All the wordlines  $R_i$  are "1" except the selected wordline which is "0"

Normally on transistors: have a lower threshold voltage (channel implant)


# Implant-Mask-Programmable NAND ROM (2)

 

4x4 bit NAND ROM array layout


- The structure is more compact than NOR array (no contacts)
- The access time is larger than NOR array access time (chain of nMOS)
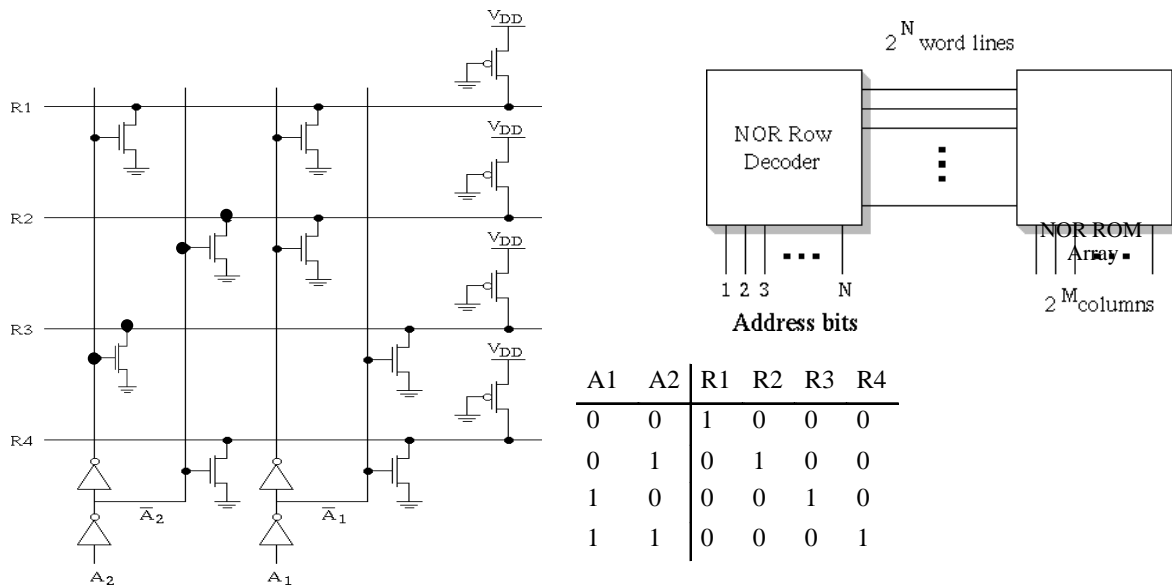
## NOR Row Address Decoder for a NOR ROM Array





- The decoder must select out one row by rising its voltage to "1" logic
- Different combinations for the address bits  $A_1A_2$  select the desired row
- The NOR decoder array and the NOR ROM array are fabricated as two adjacent arrays, using the same layout strategy
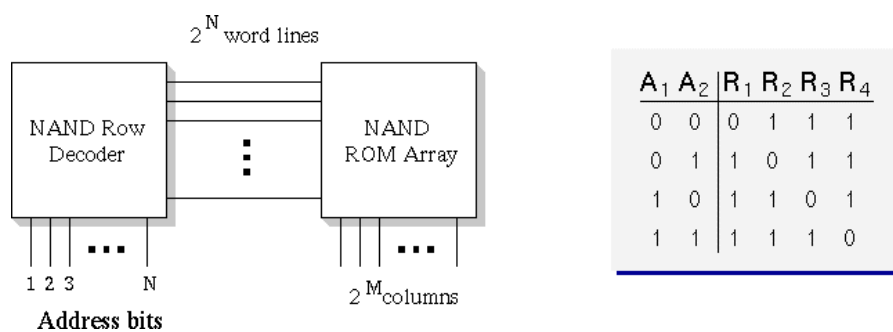
## NAND Row Address Decoder for a NAND ROM Array



- The decoder has to lower the voltage level of the selected row to logic "0" while keeping all the other rows at logic "1"
- The NAND row decoder of the NAND ROM array is implemented using the same layout strategy as the memory itself
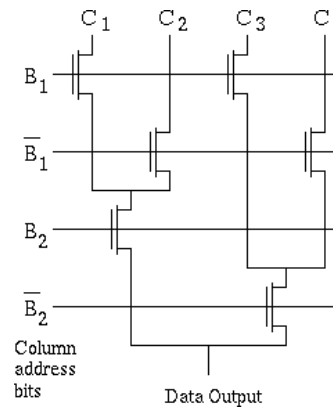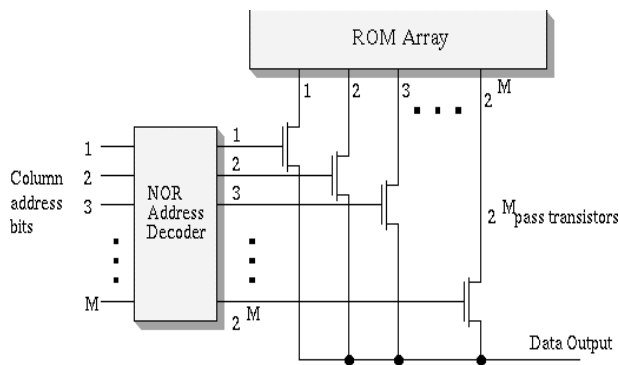
## NOR Column Address Decoder for a NOR ROM Array



NOR Address decoder +  $2^M$  pass transistors

- Large area!

Binary selection tree decoder

- No need for NOR address decoder, but are necessary additional inverters!
- Smaller area
- Drawback - long data access time

## Nonvolatile Read-Write Memories

- The [architecture is similar to the ROM structure](#)
- Array of transistors placed on a word-line/bit-line grid
- [Special transistor](#) that permits its [threshold](#) to be [altered electrically](#)
- [Programming: selectively disabling or enabling](#) some of these [transistors](#)
- Reprogramming: erasing the old threshold values and start a new programming cycle



Method of erasing:

- ultraviolet light - EPROMs
- electrically - EEPROMs
  
# EPROM (1)


The floating gate avalanche-injection MOS (**FAMOS**) transistor:

- **extra polysilicon strip** is inserted between the gate and the channel - **floating gate**
- **impact**: double the gate oxide thickness, reduce the transconductance, **increase** the **threshold voltage**
- **threshold voltage is programmable** by the trapping electrons on the floating gate through avalanche injection




Schematic symbol


# EPROM (2)

 

Avalanche injection

 

 Removing programming voltage leaves charge trapped



Programming results in higher  $V_T$

- Electrons acquire sufficient energy to become "hot" and traverse the first oxide insulator (100nm) so that they get trapped on the floating gate
- **Electron accumulation** on the floating gate is a self-limiting process that **increases the threshold voltage** (~7V)
- The trapped charge can be stored for many years
- The erasure is performed by shining strong ultraviolet light on the cells through a transparent window in the package
- The UV radiation renders the oxide conductive by direct generation of electron-hole pairs






## EPROM (3)

- The erasure process is slow (~min.)
- The erasure procedure is **off-system!**
- Programming takes several usecs/word
- Limited endurance - max 1000 erase/program cycles
- The cell is very simple and dense: large memories at low cost!
- Applications that do not require regular reprogramming
   
## EEPROM


- Provide an electrical-erasure procedure
- Modified floating-gate device, floating-gate tunneling oxide (**FLOTOX**):
  - reduce the distance between floating gate and channel near the drain
  - **Fowler-Nordheim tunneling mechanism** (when apply 10V over the thin insulator)
- Reversible programming by reversing the applied voltage (rise and lower the threshold voltage) ↓ difficult to control the threshold voltage ↓ extra transistor required as access device
- Larger area than EPROM
- More expensive technology than EPROM
- Offers a higher versatility than EPROM
- Can support  $10^5$  erase/write cycles


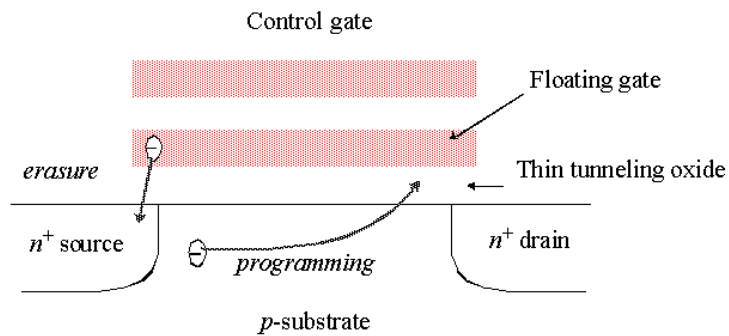
# Flash Memories

Combines the density of the EPROM with the versatility of EEPROM structures




- Programming: avalanche hot-electron-injection
- Erasure: Fowler-Nordheim tunneling (as for EEPROM cells)
- Difference: erasure is performed in bulk for the complete (or subsection of) memory chip - reduction in flexibility!
- Extra access transistor of the EEPROM is eliminated because the global erasure process allows a careful monitoring of the device characteristics and control of the threshold voltage!
- High integration density




ETOX Flash cell - introduced by INTEL
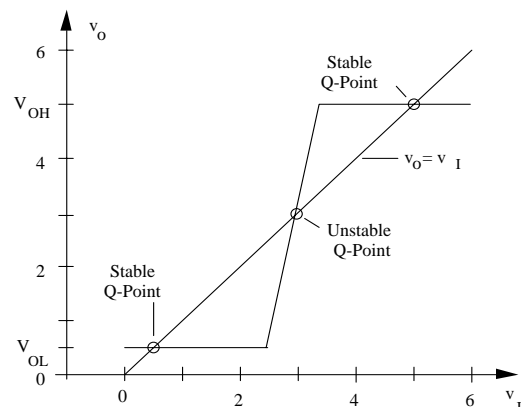  
## Static Random Access Memory - SRAM (1)

- Permit the modification (writing) of stored data bits
- The stored data can be retained infinitely, without need of any refresh operation
- Data storage cell - simple latch circuit with 2 stable states
- Any voltages disturbance  $\Downarrow$  the latch switches from one stable point to the other stable point
- Two switches are required to access (r/w) the data




# Static Random Access Memory - SRAM (2)

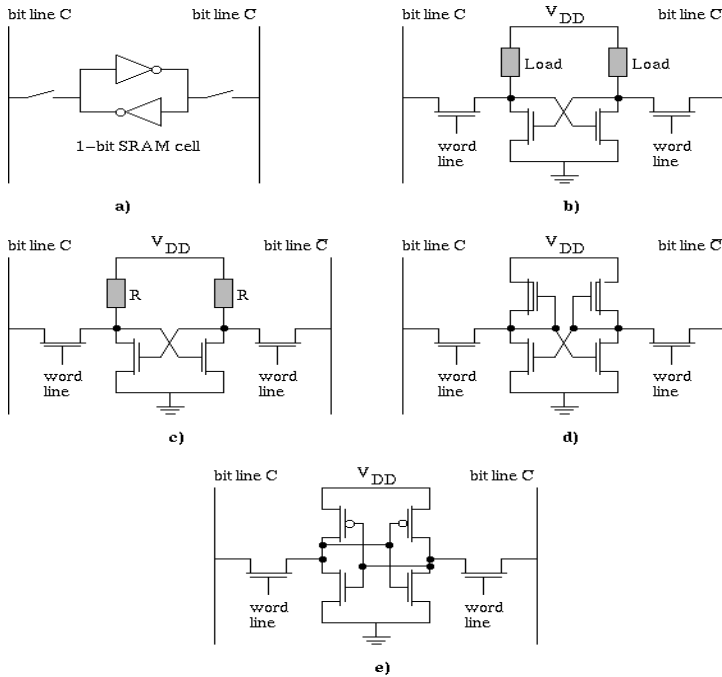

- a) general structure of a SRAM cell based on two inverter latch circuit
- b) implementation of the SRAM cell
- c) resistive load (undoped polysilicon resistors) SRAM cell
- d) depletion load NMOS SRAM cell
- e) full CMOS SRAM cell
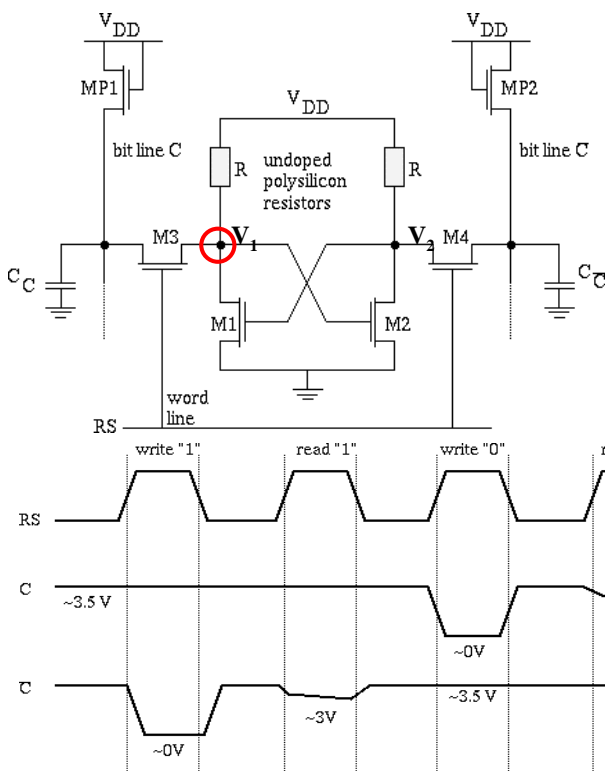
## Resistive Load SRAM Cell - Operation Principle (1)



- MP1,2 pull up transistors - charge up the large column parasitic capacitances  $C_C, C_{\bar{C}}$
- The steady-state voltage:  $V_{C_c} = V_{DD} - V_T \sim 3.5V$

○ Here we define the memory content to be located

The basic operations on SRAM cells

RS = 1 (M3, M4 on)

- Read/Write "1"
- Read/Write "0"


RS = 0 (M3, M4 off)

- data is being held

## Resistive Load SRAM Cell - Operation Principle (2)


- [Write "1" operation](#) (RS = 1 - M3, M4 on)  
 $V_{\bar{C}}$  - forced to 0 by data write circuitry,  $V_2$  decreases to 0, M1 off;  $V_1$  increases;  
Final state:  $V_1 = 1, V_2 = 0$
- [Read "1" operation](#) (RS = 1 - M3, M4 on)  
M1 off; M2, M4 on;  $V_{\bar{C}}$  - pulled down,  $V_C > V_{\bar{C}}$  read as a logic "1"
- [Write "0" operation](#) (RS = 1 - M3, M4 on)  
 $V_C$  - forced to 0 by data write circuitry,  $V_1$  goes to 0, M2 off;  $V_2$  increases to 1  
Final state:  $V_1 = 0, V_2 = 1$
- [Read "0" operation](#) (RS = 1 - M3, M4 on)  
M2 off; M1, M3 on;  $V_C$  - pulled down,  $V_C < V_{\bar{C}}$  read as logic 0

## Full CMOS SRAM Cell

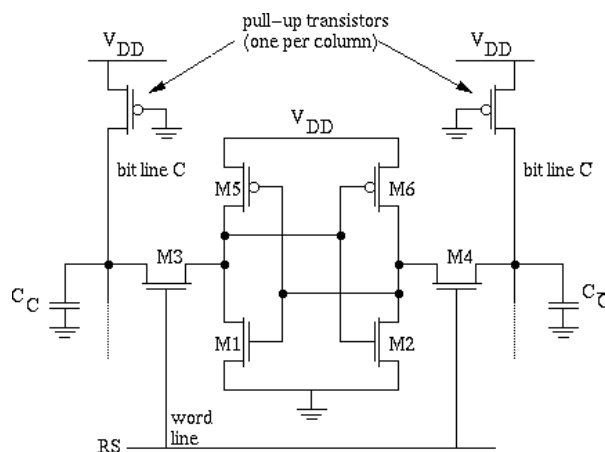


- Low-power SRAM Cell: the static power dissipation is limited by the leakage current during a switching event
- The pMOS pull-up transistors allow the column voltage to reach full  $V_{DD}$  level
- High noise immunity due to larger noise margins
- Lower power supply voltages than resistive-load SRAM cell
- Drawback: large area!

# CMOS SRAM Cell Design Strategy (1)

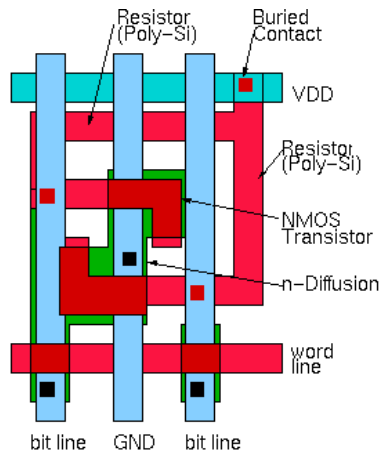

Layout of the resistive-load SRAM cell

 


Layout of the CMOS SRAM cell

# CMOS SRAM Cell Design Strategy (2)

 (1) The **data read operation** should not destroy the stored information

Assume that a logic "0" is stored in the cell ( $V_1 = 0, V_2 = 1$ : M1, M6-linear; M2, M5-off)



Design rule:

- RS = 0: M3, M4-off;
- RS = 1: M3-saturation; M4, M1-linear

$V_C$  decreases,  $V_1$  increases slowly

Condition - M2 must remain **turned off** during the data reading operation:

$$V_{1, \max} \leq V_{T,2}; I_{M3} = I_{M1} \Rightarrow$$


$$\left(\frac{W}{L}\right)_3 < \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} - 2V_{T,n})^2} \left(\frac{W}{L}\right)_1$$

A symmetrical rule is valid also for M2 and M4

# CMOS SRAM Cell Design Strategy (3)

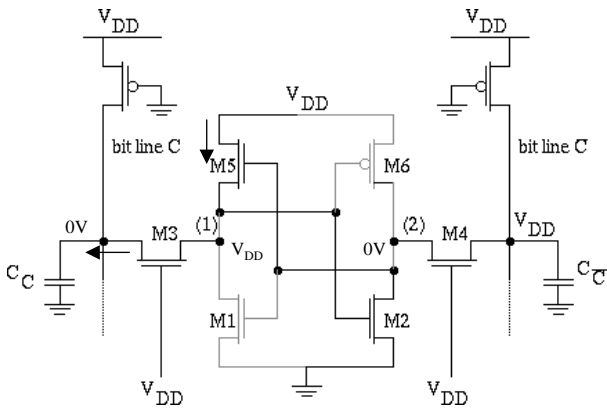(2) The cell should allow modification of the stored information during the **data write** phase

Consider the write "0" operation, assuming that "1" is stored in the cell ( $V_1 = 1, V_2 = 0$ : M1, M6-off; M2, M5-linear)



- RS = 0: M3, M4-off;
- RS = 1: M3, M4 saturation, M5-linear

In order to change the stored information:  $V_1 = 0, V_2 = 1 \Rightarrow$  M1 on and M2 off!

But  $V_2 < V_{T1}$  (previous design condition)  $\Rightarrow$  M1 cannot be switched on!  $\Rightarrow$  M2 must be switched off  $\Rightarrow V_1$  must be reduced below  $V_{T2}$

$$V_1 \leq V_{T,2}; I_{M3} = I_{M5} \Rightarrow$$


Design rule:

$$\left(\frac{W}{L}\right)_5 = \frac{\mu_n}{\mu_p} \frac{2(V_{DD} - 1.5V_{T,n})V_{T,n}}{(V_{DD} + V_{T,p})^2}$$

A symmetrical rule is valid also for M6 and M4


## SRAM Write Circuitry

$\overline{W}$	DATA	WB	$\overline{WB}$	Operation
0	1	1	0	M1-off, M2-on, $V_C$ high, $V_{\overline{C}}$ low
0	0	0	1	M1-on, M2-off, $V_C$ low, $V_{\overline{C}}$ high
1	X	0	0	M1, M2 off, $V_C, V_{\overline{C}}$ high

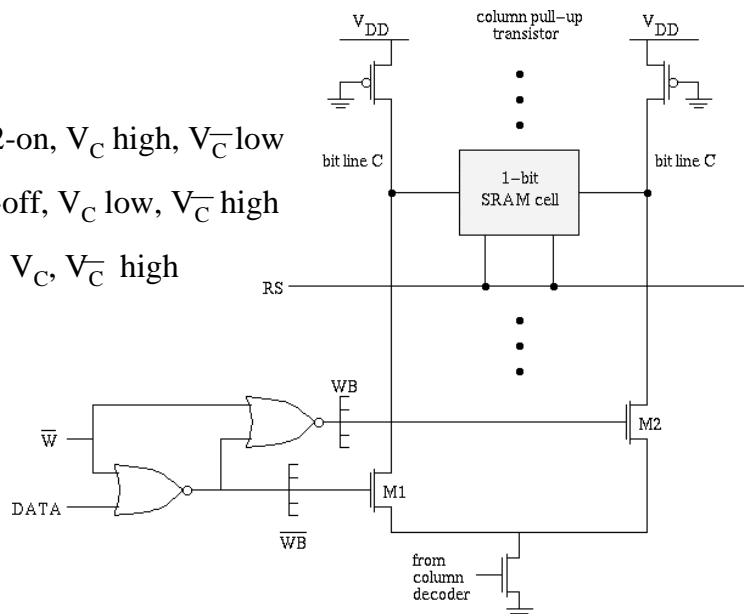

Write operation is performing by forcing the voltage level of either column (bit line) to "0"

## SRAM Read Circuitry

 

The read circuitry must detect a very small difference between the two complementary columns (sense amplifier)

$$\frac{\partial(V_{o1} - V_{o2})}{\partial(V_C - V_{\bar{C}})} = -R \cdot g_m, \text{ where } g_m = \frac{\partial I_D}{\partial V_{GS}} = \sqrt{2k_n I_D}$$


The gain can be increased by using

- active loads
- cascode configuration

Precharging of bit lines plays a significant role in the access time!

- The equalization of bit lines prior to each new access (between two access cycles)

## Dual Port SRAM Arrays

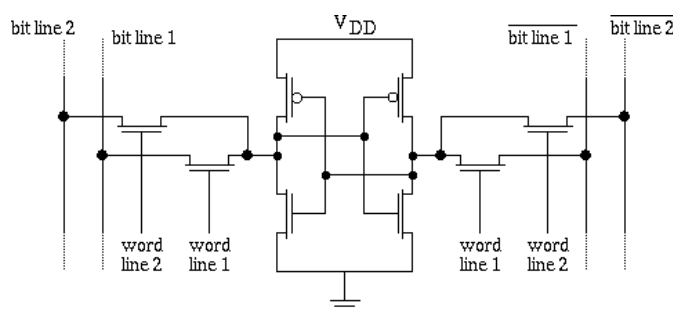

Allows simultaneous access to the same location in the memory array (systems with multiple high speed processors).

- Eliminates wait states for the processes during data read operation
- Problems can occur if:
  - two processors attempt to write data simultaneously onto the same cell
  - one processor attempts to read while other writes data onto the same cell
- Solution: [contention arbitration logic](#)

# Dynamic Random Access Memories - DRAM

(1)


## SRAM drawbacks

- large area: 4-6 transistors/bit + 4 lines connections
- static power dissipation (exception CMOS SRAM)

Need for high density RAM arrays → DRAM
 
## DRAM


- binary data is stored as charge in a capacitor
- requires periodic refreshing of the stored data
- no static power dissipation



## 4-transistor DRAM cell


- one of the earliest DRAM cells
- derived from 6 transistor SRAM cell
- two storage nodes (parasitic capacitances)
- large area
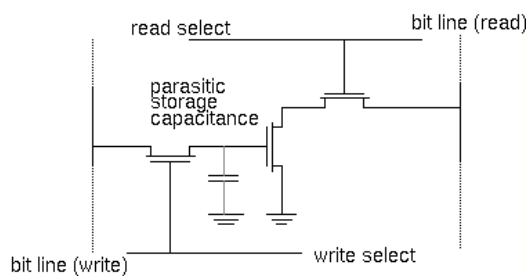
# Dynamic Random Access Memories - DRAM (2)


 
## 3-transistor DRAM cell

- 1 transistor - storage device
- 2 transistors for r/w access (switches)
- 2 r/w control lines
- 2 I/O lines




## 1-transistor DRAM cell

- 1 transistor for r/w access
- 1 explicit capacitor - information storage
- 1 r/w control line
- 1 I/O line




# Three-Transistor DRAM Cell (1)

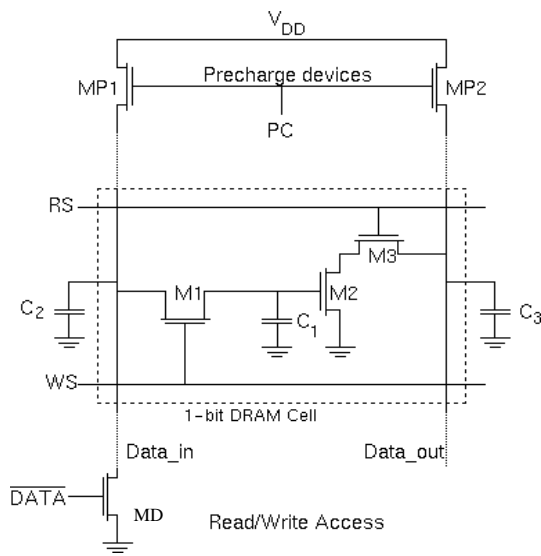

MP1, MP2 pull-up (precharge) transistors  
 M2 storage transistor (on or off depending on the charge stored in C1)  
 M1, 3 access switches  
 C2, 3 >> C1

Two phase non overlapping clock scheme  
 CLK1 - precharge events  
 CLK2 - r/w events (CLK1 - low)

# Three-Transistors DRAM Cell (2)

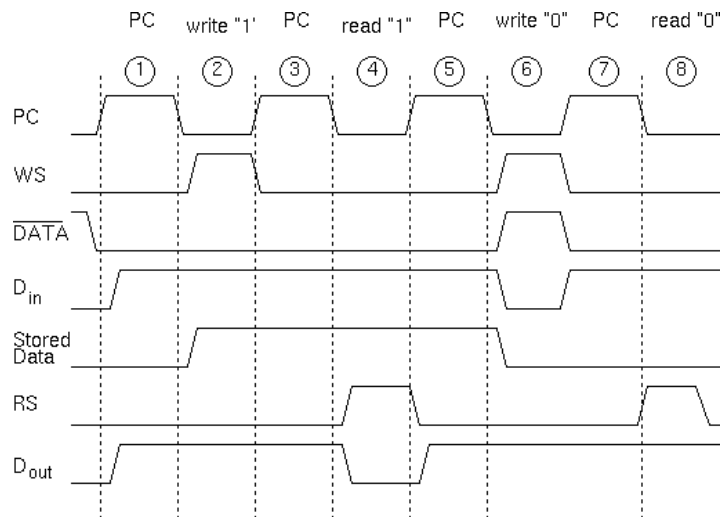


- **Every r/w operation is preceded by a precharge cycle** - C2, 3 are charged up
- Refresh operation (row): data are read, inverted and written back into the same cell location every 2-4 ms

## Three-Transistors DRAM Cell (3)

 
### WRITE 1 operation:

- Precharge: C2, C3 charged up to 1 logic level
- $\overline{\text{DATA}} = 0$ , MD off; WS = 1, M1 on  $\Rightarrow$  the charge on C2 is shared with C1
- After write operation: WS = 0, M1 off; Since C1 is charged up to 1: M2 on


 
### READ 1 operation:

- Precharge: C2, C3 charged up to 1 logic level
- RS = 1, M3 on, M2 on
- C3 discharges through M2, M3 and the falling column voltage is interpreted as a stored 1




## Three Transistors DRAM Cell (4)

### Write 0 operation:

- Precharge: C2, 3
- $\overline{\text{DATA}} = 1$ , MD on; WS = 1, M1 on  $\Rightarrow$  C2, C1 pulled to 0 through M1 and MD;
- After write operation WS = 0, M1 off; C2 is discharged to 0, M2 off

 
### READ 0 operation:

- Precharge: C2, 3
- RS = 1, M3 on; M2 off
- C3 does not discharge - the 1 logic level is interpreted as a stored 0



C1 is discharged by the leakage currents of M1 - data must be periodically read, inverted and written back!

# One-Transistor DRAM Cell (1)

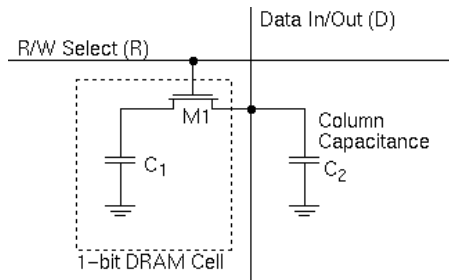



- 1 transistor M1
- 1 explicit capacitor C1: 30-100 fF, ( $C1 \ll C2$ )

Charge sharing between C2 and C1 has a key role in the r/w operations

- Data WRITE:
  - “1” - D = 1, R/W = 1 M1-on; C1 charge up to 1 level
  - “0” - D = 0, R/W = 0 M1-on; C1 discharge to 0 level
- Data READ (destructive operation):
  - Precharge C2
  - R/W = 1 M1-on; charge sharing between C1 and C2
  - Data refresh operation is required!


# One-Transistor DRAM cell (2)

  - (1) Data
- (2) Gate
- (3) Drain area
- (4) Source area
- (5) Field oxide
- (6) Capacitor plate (Poly Si)
- (7) Capacitor insulator
- (8) Storage node electrode (Poly Si)
- (9) Substrate (Si)




One Transistor DRAM cell with trench capacitor (cross-section)

## Data Read Example (1)

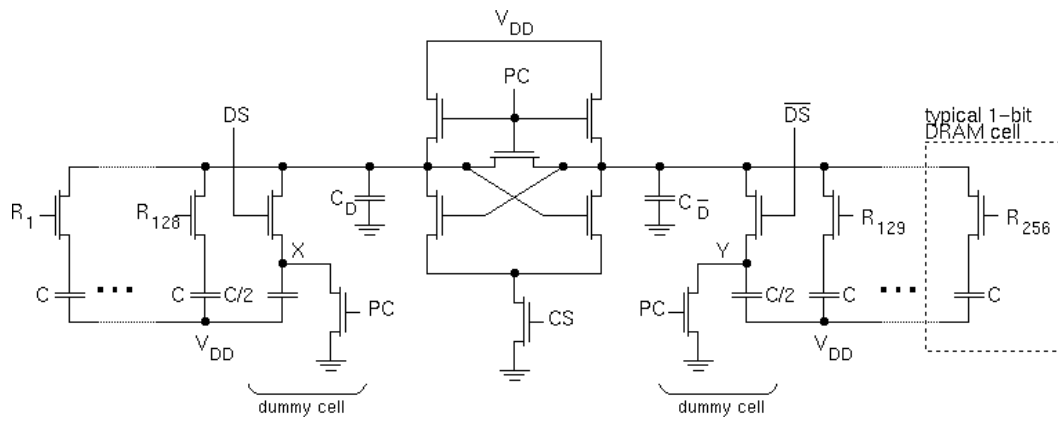


 - 256 cells per column DRAM
- The storage array is split in half
- A cross-coupled dynamic latch is used to restore the signal levels
- The dummy cell has a capacitance equal to half of the storage capacitance value



Three stages read-refresh operation


## Data Read Example (2)

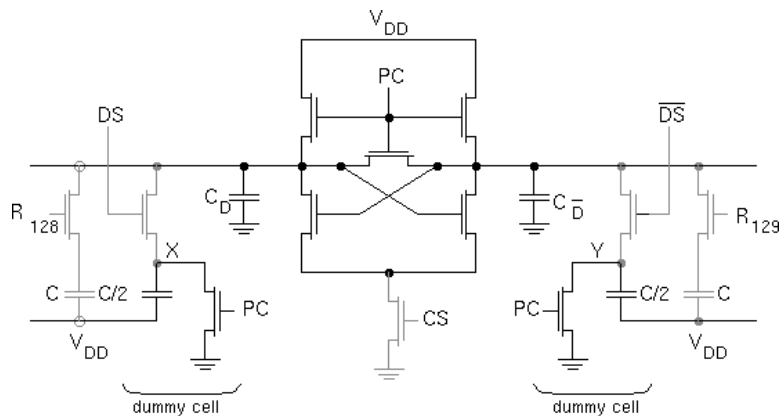

Precharge phase (1)


- Precharge devices are turned on,  $C_D$  and  $C_{\bar{D}}$  are charged up to "1" level
- The dummy nodes X and Y are pulled to "0" level
- During this phase all other signals are inactive

## Data Read Example (3)

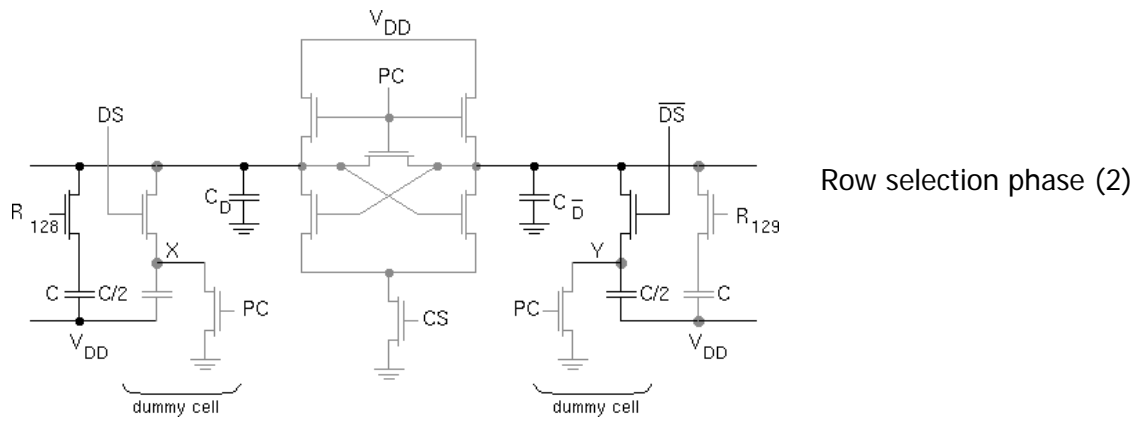

- One of the 256 word lines is raised to "1" (cell  $R_{128}$  is selected)
- The corresponding dummy cell on the other side is also selected (right)
- Charge sharing between the selected cell and  $C_D$  (depending on the value stored by cell "0" or "1") and between dummy cell and  $C_D$
- Voltage level is detected through the charge sharing

## Data Read Example (4)

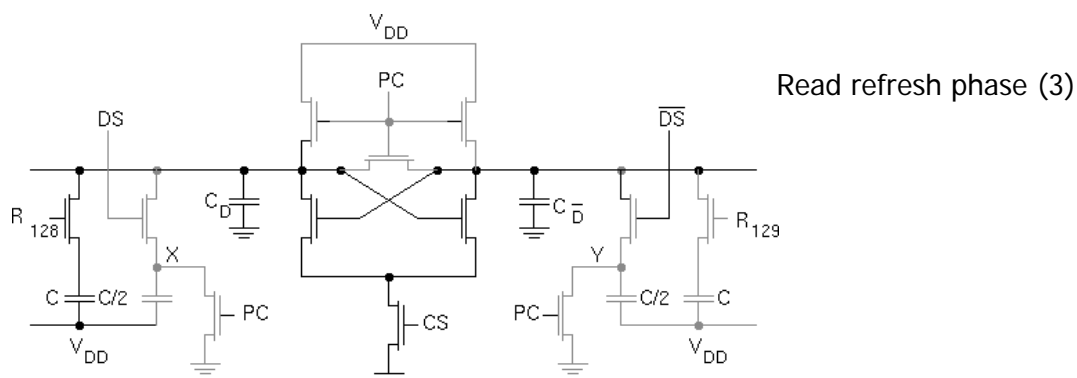

- Performed during the active phase of the CS (column-select signal)
- The slight voltage difference between the two half-column is amplified and the latch forces the two half-columns into opposite states
- The voltage level on the accessed cell is restored

## DRAM Architectures

Name	Feature	Die size increase	Frequency (system level)	Application
<b>DRAM</b>	Fast page mode	-	25MHz	Main memory
<b>VRAM</b>	DRAM+SAM	50%	40MHz	Viedo display buffer
<b>EDO</b>	DRAM with modofied CAS	0%	40-50MHZ	Main memory, low-end graphic memory
<b>SDRAM</b>	Sync.DRAM+Register (Latch)	0-10%	60-150MHz	Main memory in workstations, high end PCs, middle range graphic memory
<b>SGRAM</b>	SDRAM+Block write+ WPB	10%	60-150MHz 3Gb/s	High-end memory
<b>CDRAM</b>	Sync.DRAM+SRAM+ DTB	7-10%	66MHz	Low-end PC
<b>RDRAM</b>	Sync.DRAM+Raambus I/O	12-15%	250MHz	High-end PC, graphic memory
<b>3D-RAM</b>	Sync.DRAM+SRAM+ SAM+ALU	?	400Mb/s ext, 1.6 Gb/s int	High-end graphic memory
<b>EDRAM</b>	DRAM + SRAM	?	?	Low-end PC
<b>SVRAM</b>	Sync.DRAM+SAM	50%	100MHz	High-end graphic memory
<b>WRAM</b>	VRAM with localized SAM	<40%	66MHz	Middle to high-end graphic memory

## Summary

- the memory architecture has a major impact on the ease of use of the memory, its reliability and yield, its performance and power consumption;
- [memories are organized as arrays of cells](#); an individual cell is addressed by a [column and row address](#);
- the memory cells should be designed so that a maximum signal is obtained in a minimum area; the cell design is dominated by technological considerations and most of the improvement in density results from scaling and advanced manufacturing processes;
- we have discussed cells for read-only memories (NOR and NAND ROM), nonvolatile memories (EPROM, EEPROM and FLASH) and read-write memories (SRAM and DRAM)
- the [peripheral circuitry is very important](#) to operate the memory in a reliable way and with reasonable performance; decoders, sense amplifiers and I/O buffers are an integral part of every memory design;